

B TECH
(SEM IV) THEORY EXAMINATION 2017-18
Network Analysis and Synthesis

Time: 3 Hours

Total Marks: 100

Note: 1. Attempt all Sections. If require any missing data; then choose suitably.

SECTION A


1. Attempt *all* questions in brief. 2 x 10 = 20

- a. Write down the properties of a tree in the graph.
- b. If $Z_L = 4 + 2j$, what should be the value of Z_{th} for maximum power transfer.
- c. Write down the limitation of Superposition Theorem.
- d. If a network contains B branches, and N nodes, then the number of mesh current equations should be _____.
- e. What are transients and why are they produced.
- f. Determine the time constant of series RL circuit in which a constant supply of 100V is connected across the series combination of resistance of 4K Ω and inductance of 0.01mH
- g. Define complex frequency.
- h. Define Driving point function.
- i. Write down the properties of Hurwitz polynomial.
- j. What are the limitations of Foster forms?

SECTION B

2. Attempt any *three* of the following: 10 x 3 = 30

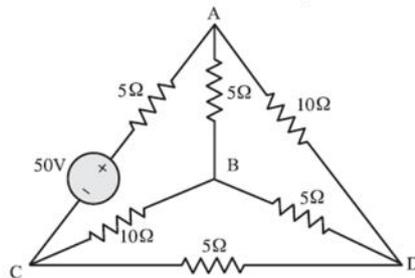- a. (i) Find out the number of possible trees for the figure given below:



- (ii) Obtain the oriented from the given Cut-set matrix:

$$[Q] = \begin{bmatrix} 1 & 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 1 & 0 \\ 1 & 0 & 0 & 1 & 0 & 0 & 1 \\ 0 & 1 & 0 & 0 & 1 & 0 & 1 \end{bmatrix}$$

- b. Find the expression of the current $i(t)$ in the circuit of figure 8 assuming that the switch is opened at $t=0$, the steady state having already reached before that.



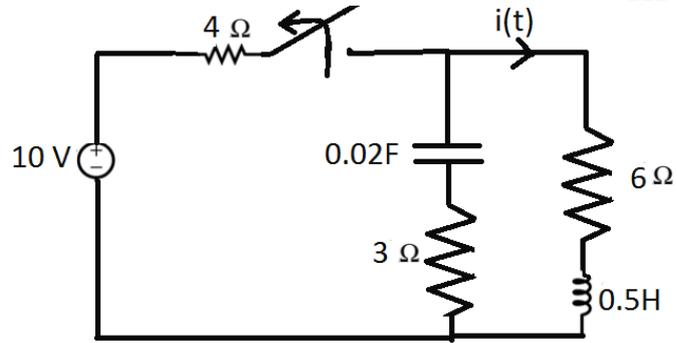


Figure 8

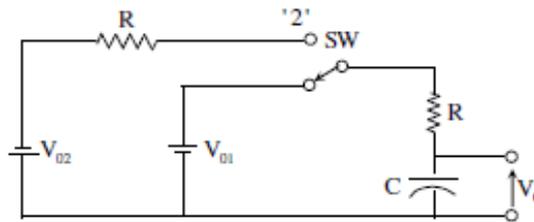- c. The switch SW shown in the circuit is kept at position '1' for a long duration. At $t = 0+$, the switch is moved to position '2'. Assuming $V_{02} < V_{01}$, find the voltage $V_C(t)$ across capacitor in the figure given below:



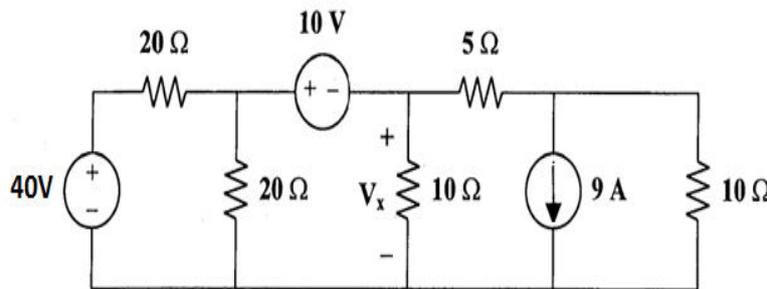- d. Explain the concept of duality. Find the dual of the network shown in figure 1.




- e. Define Sternstest. Why it is used? Explain the process involved in Stern test.


SECTION C

3. Attempt any *one* part of the following: 10 x 1 = 10

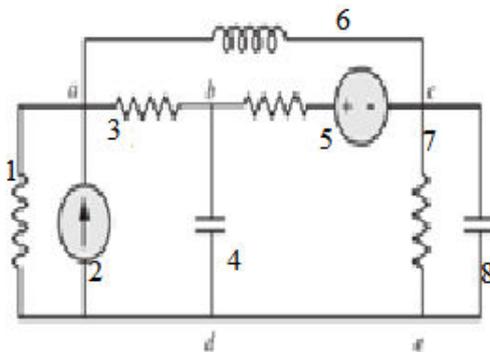- (a) Write down the Cut-set and Tie-set matrix for the circuit given in fig. Consider 3, 5 and 4 as twigs. Also write down its Impedance Matrix.




- (b) For the network shown in the figure below, draw the oriented graph and create the tie-set matrix. Use this matrix to calculate current flowing through 5V source.

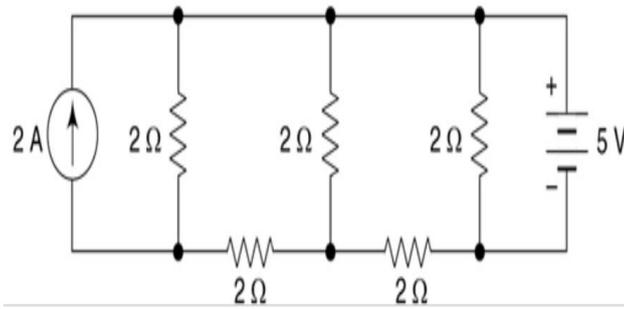


4. Attempt any *one* part of the following: 10 x 1 = 10

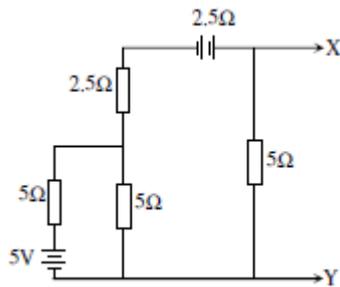(a) Obtain the Thevenin's equivalent circuit across the terminals X and Y in the circuit shown below:




(b) For the given figure, the Norton equivalent circuit is to be determined across terminal AB.

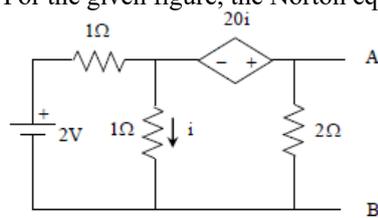


5. Attempt any *one* part of the following: 10 x 1 = 10

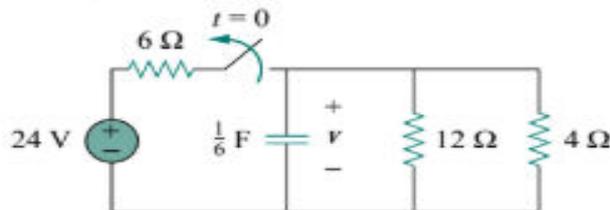(a) For the given circuit, find $v(0^+)$, $dv(0^+)/dt$, $d^2v(0^+)/dt^2$ & $v(\infty)$.




(b) Find the expression for capacitive voltage for $t > 0$ and initial energy which is stored in the capacitor.

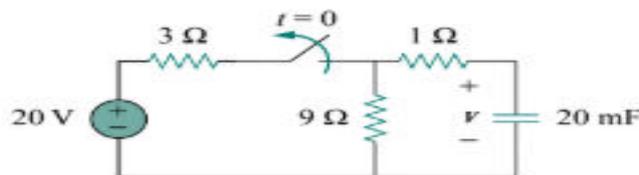


6. Attempt any *one* part of the following: 10 x 1 = 10

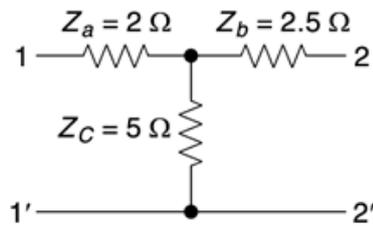(a) Find the equivalent π -network for the T-network shown in the Fig.



- (b) Find the equivalent T -network for the π -network shown in the Fig.

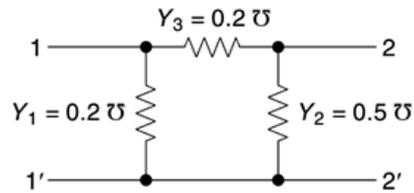

7. Attempt any *one* part of the following: 10 x 1 = 10

- (a) How the function can be identified as a positive real function? Explain with a suitable example.
- (b) Differentiate between Foster and Cauer forms and also write down the steps to obtain Foster-I and Foster-II forms.