

5. Attempt any two parts of the following: (10×2=20)

a) What is the difference between active and passive filters?
Design a constant K type band pass filter section to be terminated in 600 Ω resistance having cut-off frequencies of 2 kHz and 5 kHz.

b) Check whether the given function is positive real or not.

$$(s^3+5s^2+9s+3)/(s^3+4s^2+7s+9)$$

c) Define low pass, high pass, and band –elimination filters with the help of their attenuation characteristics.

—x—

Printed Pages :4



1214

383

NEE-402

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 121410

Roll No.

--	--	--	--	--	--	--	--	--	--

B.Tech. (Semester-IV)

SPL. THEORY EXAMINATION, 2014-15

NETWORK ANALYSIS AND SYNTHESIS

Time : 3 Hours]

[Total Marks : 100

Note: Attempt all questions. All questions carry equal marks.

1. Attempt any four parts of the following: (5×4=20)
- a) Define with suitable example: (i) Planar graph (ii) Incidence matrix (iii) Twigs (iv) Chord.
- b) Draw the oriented graph of network given in fig1. & write the incidence & reduced incidence matrix.

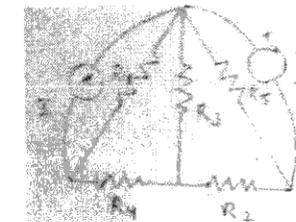


Fig. 1

121410]

(4)


1,650

121410]

(1)

[Contd...

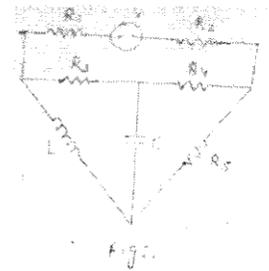
c) Write the principle of duality & draw the dual of the network given below.



- d) List out the various properties of complete incidence matrix.
- e) Show that f-cutset and f-loop matrix is orthogonal to each other.
- f) Define the term: Tree, Co-tree and link.

2. Attempt any two parts of the following: (10×2=20)

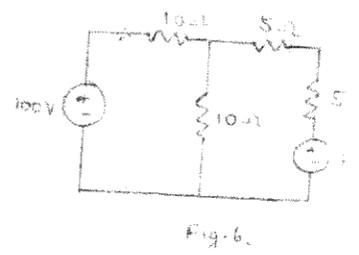- a) State and prove maximum power transfer theorem for A.C circuits.
- b) State Millman's theorem and compensation theorem with a suitable example.
- c) State tellegen's theorem. Find the value of source E_2 using tellegen's theorem if the power absorbed by E_2 is 120 W in fig below.



121410] (2) 1,650

3. Attempt any two parts of the following: (10×2=20)

- a) (i) Explain the concept of complex frequency.
- (ii) Explain the concept of poles and zeros of a network function.
- b) (i) Calculate the range of K for which the system is given by the characteristics equation.

$$S^3 + 7S^2 + 10S + K = 0$$

- (ii) Check the stability of the system with characteristics equation.

$$S^5 + 4S^4 + 8S^3 + 8S^2 + 7S + 4 = 0$$

- c) Find the driving point impedance of the network shown in fig below. Find the pole and zero of the network and locate them in the s-plane.



4. Attempt any two parts of the following: (10×2=20)

- a) The ABCD parameters of a two port n/w are $A=2$, $B=5$, $C=1/3$, $D=4/3$. Determine z, y & h- Parameters.
- b) Obtain the Z-parameters of the network in terms of T-parameters.
- c) Show that the overall transmission parameter matrix for cascade two 2-port networks is simply the matrix product of transmission parameters for each individual 2-port network in cascade.

121410] (3) 1,650