

Printed Pages—6

TEE—402

(Following Paper ID and Roll No. to be filled in your Answer Book)

**PAPER ID : 2052**

Roll No.

--	--	--	--	--	--	--	--	--	--

**B.Tech.**

FOURTH SEMESTER EXAMINATION, 2005-2006

**NETWORK ANALYSIS AND SYNTHESIS**

Time : 3 Hours


Total Marks : 100

- Note :**
- (i) Attempt *ALL* questions.
  - (ii) All questions carry equal marks.
  - (iii) In case of numerical problems assume data wherever not provided.
  - (iv) Be precise in your answer.

1. Attempt *any three* parts of the following :  $(6\frac{2}{3} \times 3 = 20)$

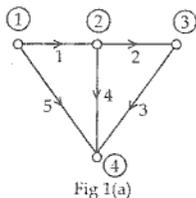- (a) Differentiate the terms "Cut-set" and "Tie-set" related to a linear graph.

Write the properties of incidence matrix and also obtain the incidence matrix of the graph shown in fig 1(a)



001\_01

- (b) In graph theory, derive the relation among submatrices of  $A$ ,  $B$  and  $Q$ , where  $A$ ,  $B$  and  $Q$  have their usual meanings.
- (c) A resistive network is shown in fig 1(c), write corresponding tie-set matrix and obtain KVL equation using graph theory.

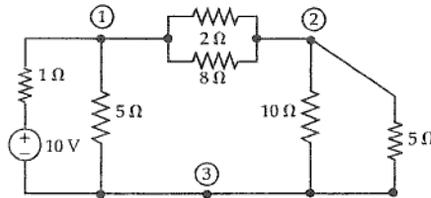


Fig. 1(c)

- (d) Show the cut-sets for the graph of the network shown in fig 1(d) and develop the fundamental cut-set matrix.

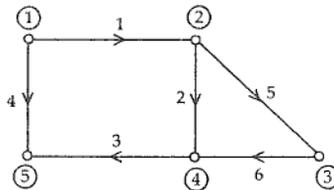


Fig. 1(d)

- (e) Prove that given circuits shown in fig 1(e) (i) and 1e(ii) are duals of each other. Use graph theory only.

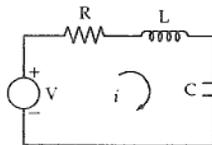


Fig. 1(e)(i)

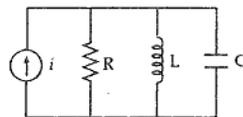


Fig. 1(e)(ii)

+

2. Attempt *any three* parts of the following :  $(6\frac{2}{3} \times 3 = 20)$

- (a) In the network shown in fig 2(a), find the current through capacitor using principle of superposition.

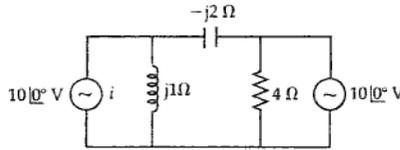


Fig. 2 (a)

- (b) Find the Thevenin's equivalent circuit for the network given in fig 2(b) across A and B.

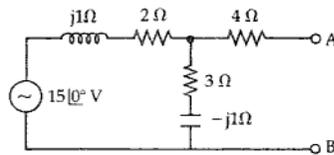


Fig. 2 (b)

- (c) In the network shown in fig 2(c), find the value of  $R_L$  which results in maximum power transfer. Also find maximum power.

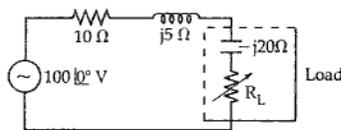


Fig. 2 (c)

- (d) State the Tellegen's theorem and verify it for the network shown in fig 2(d).

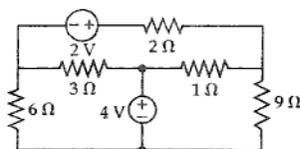


Fig. 2 (d)

- (e) Verify Reciprocity theorem of the network shown in fig 2 (e) and find  $V_x$ .

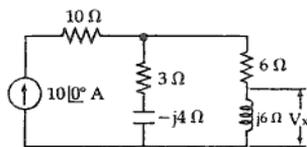


Fig. 2 (e)

3. Attempt *any two* parts of the following : (10x2=20)

- (a) Enlist the necessary conditions for transfer function in terms of pole and zero locations. Draw the pole-zero diagram of the given function and obtain time domain response using if.

$$I(S) = \frac{2S}{(S+1)(S^2+2S+4)}$$

- (b) (i) Using Routh - Hurwitz criterion, check the stability of the following polynomials.

$$P(S) = S^6 + S^5 + 3S^4 + 3S^3 + 3S^2 + 2S + 1$$

(ii)  $P(S) = S^4 + 20KS^3 + 5S^2 + 10S + 15 = 0$

is a characteristic equation of control system. Find the range of K for the system to be stable.

- (c) Draw the Bode plot of the following transfer function having unity feedback.

$$G(S) = \frac{50}{S(1+S)(5+S)(10+S)}$$

Find gain cross over and phase cross-over frequency.

4. Attempt *any two* parts of the following : (10x2=20)

- (a) Find Y-parameters of the network shown in fig 4(a) and check whether the circuit is symmetric and reciprocal or not.

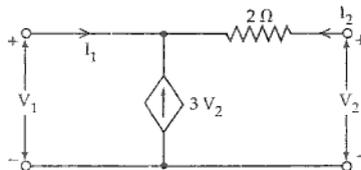


Fig. 4(a)

Also hence find h-parameters of the network.

- (b) A 2-port network made up of passive linear resistors is fed at port 1 by an ideal voltage source of  $V$  volts. It is loaded at port 2 by a resistance  $R$ :
- With  $V = 10$  volts and  $R = 6\Omega$ , currents at ports 1 and 2 were 1.44 A and 0.2A respectively.
  - With  $V = 15$  volt and  $R = 8\Omega$ , the current at port 2 was 0.25 A. Determine  $\pi$  equivalent circuit of 2-port network.
- (c) For the two part network shown in fig 4(c), find h parameters and hence find ABCD parameters.

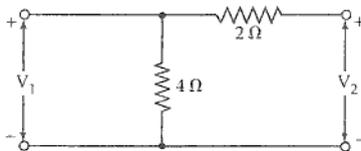


Fig. 4(c)

5. Attempt *any three* parts of the following :  $(6\frac{2}{3} \times 3 = 20)$

- (a) Enlist the properties of an LC immittance driving point function. Obtain the driving point impedance in Laplace form of the given network across a-b shown in fig 5(a).

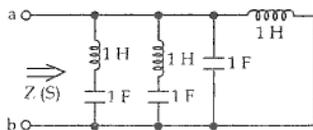


Fig. 5 (a)

- (b) An impedance function is given by

$$Z(S) = \frac{2(S+1)(S+3)}{(S+2)(S+4)}$$

Find the R-L representation of Foster first form.

- (c) List and explain the properties of a passive filter.
- (d) A T-section low pass filter has series inductance 80 mH and shunt capacitance  $0.022\mu\text{F}$ . Determine the cut-off frequency and nominal design impedance. Also design an equivalent  $\pi$ -section.
- (e) A series LCR type band-stop filter has  $R = 1.5 \text{ k}\Omega$ ;  $L = 140 \text{ mH}$  and  $C = 300 \text{ pf}$ . Find the
- (i) Resonant frequency and
  - (ii) Bandwidth. Also find the cut-off frequencies.

- o O o -