



Printed Pages : 4

EE - 607

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 2028

Roll No.

| | | | | | | | | | | | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|
| | | | | | | | | | | | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|

B. Tech.

(SEM. VI) EXAMINATION, 2006-07

FUNDAMENTALS OF POWER ELECTRONICS

Time : 3 Hours]

[Total Marks : 100

Note : Attempt all five questions. All questions carry equal marks.

- 1 Attempt any **four** parts of the following : **5×4=20**
- (a) Discuss the difference between :
 - (i) Triac and Thyristor
 - (ii) MOSFET and IGBT.
 - (b) Explain the differences in the gating requirements of thyristor and transistor.
 - (c) Draw the thyristor voltage and current waveforms during turn-on and turn-off processes.
 - (d) What are different possible configurations of a single-phase voltage controller ? Also, list some of industrial applications of the ac voltage controllers.
 - (e) Discuss the merits of controlling the heater power by a Triac using integral cycle control over the phase-angle control.
 - (f) Discuss the functions of diodes in antiparallel with thyristors in the inverter circuits.

- 2 Attempt any **four** parts of the following : **5×4=20**

V-2028]

1

[Contd...

- (a) Explain the control of a chopper output voltage using variable frequency system.
- (b) Discuss the effect of source inductance in a fully controlled single phase bridge rectifier.
- (c) Explain the difference between line-commutated inverters.
- (d) Explain Pulse Width Modulation? List the different PWM techniques.
- (e) For a three phase induction motor, explain why V/f ratio is maintained constant for operation below the base speed.
- (f) Explain the static V-I characteristics of a Triac.

3 Attempt any **two** parts of the following : **10×2=20**

- (a) A single-phase fully controlled rectifier bridge delivers power to a resistive load R. Sketch the time variation of source voltage V_s , output voltage, output current and voltage across one pair of SCRs. Show that average output Voltage V_0 is

$$V_0 = \frac{\sqrt{2} V_s}{\pi} (1 + \cos \alpha)$$

- (b) Describe modes of operation of modified Mc-Murray Bedford half-bridge single-phase inverter. Also draw its relevant voltage and current waveforms.
- (c) Describe the principle of burst firing control for a single-phase ac voltage controller, for a resistive load. Show that its power factor is given by,

$$\left[\frac{1}{\pi} \left\{ (\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right\} \right]^{1/2}$$

4 Attempt any **two** parts of the following : **10×2=20**

- (a) Show that the fundamental rms value of per-phase output voltage of low-frequency for an m-pulse cycloconverter is given by,

$$V_{0r} = V_{ph} \left(\frac{m}{\pi} \right) \sin \left(\frac{\pi}{m} \right)$$

Also express V_{0r} in terms of voltage reduction factor.

- (b) A three-phase fully controlled bridge converter is connected to a pure resistive load. Show that the average output voltage is given by,

$$V_{0r} = \frac{6V_L}{\sqrt{2} \pi} \cos \alpha \text{ for } \alpha < \frac{\pi}{3} \text{ and}$$

$$V_0 = \frac{6V_L}{\sqrt{2} \pi} \left[1 + \cos \left(\alpha + \frac{\pi}{3} \right) \right] \text{ for } \frac{\pi}{3} < \alpha < \frac{2\pi}{3}$$

where V_L is rms value of line Voltage.

- (c) A single-phase fully controlled bridge converter is connected to ac supply of $320 \sin 314 t$ Volt and 50 Hz. It operates at a firing angle of $\frac{\pi}{4}$ rad. The total load current is maintained constant at 6A and the load voltage is 140V. Calculate the source inductance, angle of overlap and the load resistance.

5 Attempt any **two** parts of the following : **10×2=20**

- (a) Describe the following :
- (i) Static chopper based resistance control method for the speed control of a three-phase induction motor.

- (ii) Explain operation of multi quadrant chopper.
- (b) A single-phase voltage controller has resource voltage 230V at 50Hz and a pure inductive load of 5Ω
Calculate :
- (i) the control range of firing angle
 - (ii) the maximum value of rms load current,
 - (iii) the maximum value of $\frac{di}{dt}$ that may occur in the thyrister.
- (c) Explain operation of single phase half controlled bridge converter fed separately excited dc motor. Draw waveforms of load voltage, load current and source current.
-