



Printed Pages : 4

TEE – 603

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 2061

Roll No.

--	--	--	--	--	--	--	--	--	--

B. Tech.

(SEM. VI) EXAMINATION. 2007

POWER ELECTRONICS*Time : 3 Hours]**[Total Marks : 100*

Note : Answer all the five questions. All questions carry equal marks.

- 1 Answer any **four** parts of the following : **5×4=20**
- (a) List specifications of a power electronic switch.
 - (b) List ac to dc and ac to ac power electronic converters and draw their output.
 - (c) Explain switching characteristics of a power transistor.
 - (d) Draw V-I characteristics of a GTO and explain its operation.
 - (e) Draw two transistor model of a SCR and explain its turn-on mechanism. Why does SCR not turn-on in reverse biased condition ?
 - (f) Compare power transistor, MOSFET and IGBT with reference to power switching applications.

2 Answer any two parts of the following : 10×2

- (a) For the circuit shown in fig 2(a) the operating frequency is 2 kHz and the required dv/dt is $100V/\mu$ sec. If the discharge current be limited to 100A, calculate
- (i) the values of R_s and C_s
 - (ii) the power loss in the snubber.

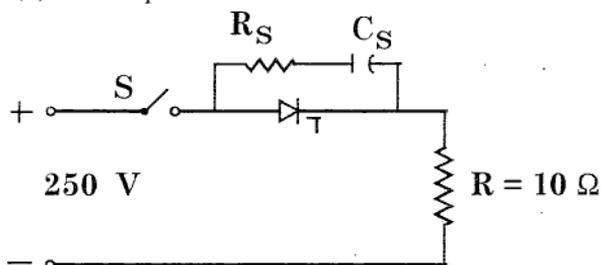


Fig. 2(a)

- (b) Why does unequal voltage sharing take place among series connected thyristors during steady state and dynamic state? How is equal voltage sharing obtained in both the states?
- (c) Discuss control strategies for operation of choppers. Why is time ratio control (TRC) preferred?

In a step down chopper feeding a resistive load, the average output voltage is 109 V. The voltage drop across the chopper switch when it is ON is 2 V. If the load resistance be 10 ohm and frequency of operation be 2kHz. For duty ratio of 0.5, calculate :

- (i) dc input voltage to the chopper
- (ii) the rms output voltage
- (iii) chopper efficiency
- (iv) input resistance of the chopper.

3 Answer any **two** parts of the following : **10×2=20**

- (a) Explain operation of a single phase fully controlled bridge converter feeding a highly inductive load. Draw wave forms of output voltage, load current and source current. What happens when the source has inductance and discuss its effect on performance of the converter.
- (b) Explain operation of a 3-phase half wave controlled converter feeding a highly inductive load making current continuous and draw load voltage waveform. Derive an expression for dc output voltage.
- (c) Draw circuit diagram of a single phase dual converter and explain its working in continuous current mode of operation. How are the firing angles of both converters decided? Discuss the need of centre tapped inductor.

4 Answer any **two** parts of the following : **10×2=20**

- (a) A single phase full wave ac regulator feeds a pure resistive load. Derive an expression for output voltage.

A single phase, 220 V, 1 KW electric room heater is connected across 220 V ac supply through a TRIAC. For a delay angle of 90° calculate the power dissipated by the heater element.

- (b) Draw a circuit diagram and explain the working of static on load tap changer for transformers.
- (c) Explain working of a single phase bridge type cycloconverter. Draw output voltage waveform for output frequency 50% of the input frequency for resistive load.

- 5 Answer any **two** parts of the following : **10×2=20**
- (a) Explain operation of a single phase full bridge inverter. Draw waveshapes of output current when :
- (i) load is pure resistive
 - (ii) load is pure inductive
 - (iii) load is R-L-C underdamped. Justify about the waveshape.
- (b) Explain operation of a three phase bridge inverter employing 120° mode of operation. Draw waveforms of phase voltages and any one line voltage assuming star-connected resistance load.
- (c) Explain operation of three phase current source inverter and mention its advantages over voltage source inverter. Give its applications.
-