

Printed Pages : 4



EEE-402

(Following Paper ID and Roll No. to be filled in your Answer Book)

**PAPER ID : 121406**

Roll No.

--	--	--	--	--	--	--	--	--	--

**B. Tech.**

(SEM. IV) THEORY EXAMINATION, 2014-15  
**NETWORK ANALYSIS & SYNTHESIS**

Time : 3 Hours]

[Total Marks : 100

Note : Attempt all questions.

1 Attempt **any TWO** parts of the following:  $10 \times 2 = 20$ 

- (a) Explain the followings matrices taking a suitable example:  
 (i) Reduced Incidence Matrix  
 (ii) Basic Cutset Matrix  
 (iii) Basic Tieset Matrix
- (b) Derive the KCL and KVL using network graph variables.
- (c) Explain the concept of duality. Find the dual of the network shown in figurel.

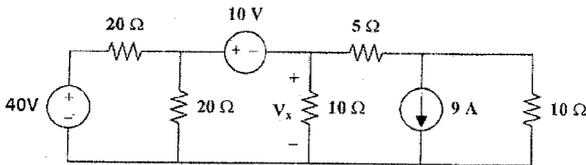


Fig. 1

2 Attempt **any FOUR** parts of the following.  $5 \times 4 = 20$ 

- (a) Find the current  $I$  and voltage  $V_{ab}$  in figure2.

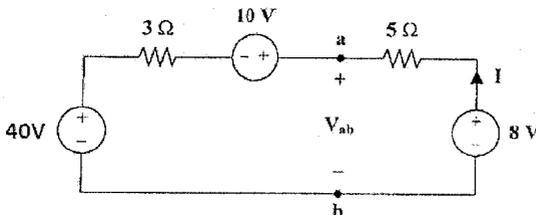



Fig. 2

121406]


1

[ Contd...

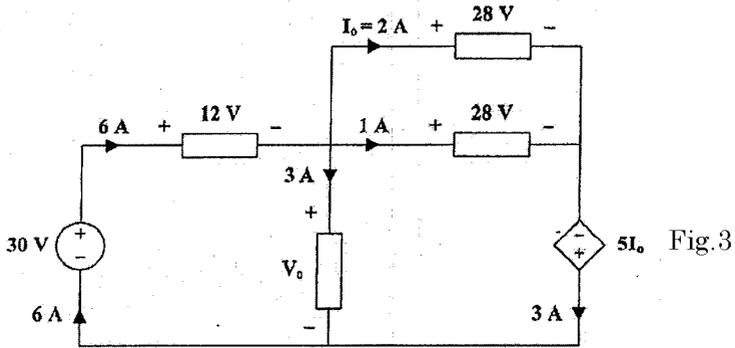
- (b) Derive the maximum power transfer theorem for the case when the source impedance is complex and the load is variable with its power factor being unity.
- (c) Find the voltage  $V_o$  in figure 3 below.



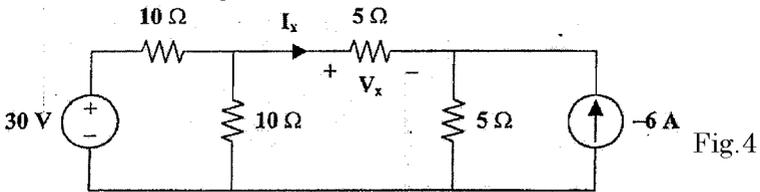- (d) Find the current  $I_x$  through the 5 ohm resistor using Thevenin's theorem in figure 4.



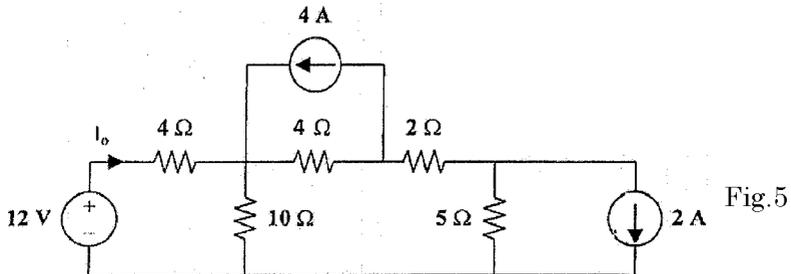
- (e) Find the current  $I_o$  using source transformation in figure 5.



- (f) State and prove the Tellegen's theorem.


3. Attempt **any TWO** parts of the following. **10×2=20**

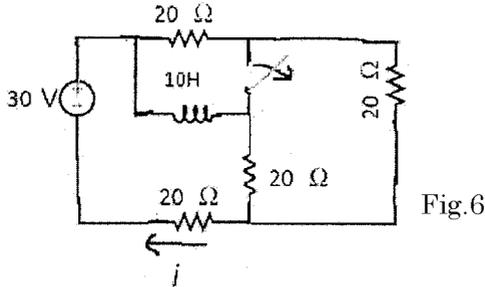- (a) (i) In the circuit shown in figure 6, the switch is kept closed for a long time and is then opened at  $t=0$ .




Find the values of current  $i$  just before opening the switch ( $t = 0^-$ ) and just after opening the switch ( $t = 0^+$ ).

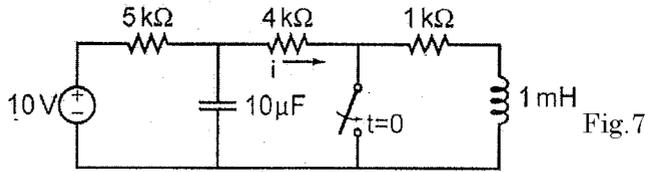
- (ii) In the figure7 shown, the ideal switch has been open for a long time. If it is closed at  $t=0$ , then find the magnitude of current (in mA) through the  $4k\Omega$  resistor at  $t=0^+$ ?



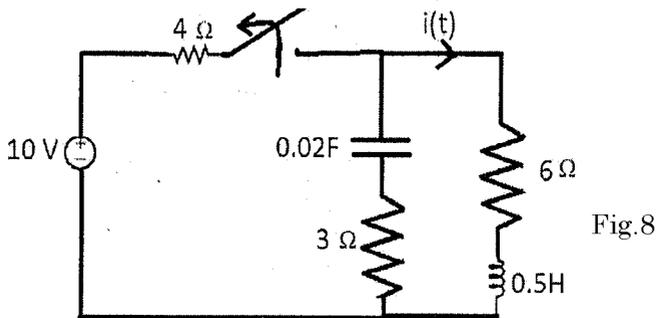
- (b) Find the expression of the current  $i(t)$  in the circuit of figure 8 assuming that the switch is opened at  $t=0$ , the steady state having already reached before that.



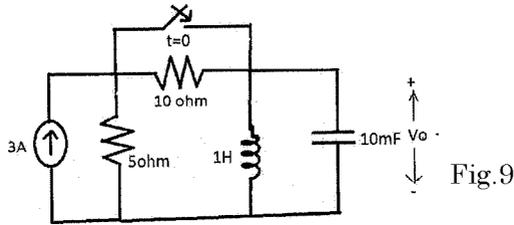- (c) Find the voltage  $V_o$  in the circuit of figure 9. The switch was open for a long time before it was closed at  $t=0$ .



- 4 Attempt **any FOUR** parts of the following: **5×4=20**
- Write the necessary conditions for the existence of transfer functions giving a suitable example.
  - What is meant by reciprocal and symmetric networks? Explain with the help of an example.
  - Derive the condition of reciprocity and symmetry for h-parameters.
  - Prove that if two 2-port networks are connected in cascade, the transmission parameter matrix of the composite two port network is the product of the two individual transmission parameter matrices.
  - Find the Y and h parameters of the network shown in figure 10.

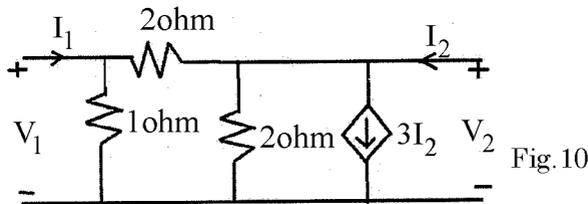

- (f) Prove that the star delta conversion does not bring any change in the Z parameter matrix for the case of a resistive network.
- 5 Attempt **any TWO** parts of the following. **10×2= 20**

(a) Given 
$$Z(s) = \frac{10(s^2 + 4)(s^2 + 6)}{s(s^2 + 5)}$$

- Find the Foster I and Cauer II forms of network.
- Explain the properties of positive real functions, LC functions and R-L functions.
- What is image parameter? Derive its expression. What are active and passive filters? Explain the advantages of active filters.