

Paper Id:

1	3	1	3	1	7
---	---	---	---	---	---

Roll No.

--	--	--	--	--	--	--	--	--	--

B.TECH
(SEM VI) THEORY EXAMINATION 2018-19
DIGITAL MEASUREMENT TECHNIQUES

Time: 3 Hours**Total Marks: 70****Note:** Attempt all Sections. If require any missing data; then choose suitably.**SECTION A**

- 1. Attempt all questions in brief. 2 x 7 = 14**
- a. Differentiate between accuracy and precision
 - b. What is the function of zero level comparator?
 - c. What do you understand by Gating error?
 - d. What is the drawback of Fast-Low frequency measurement method?
 - e. Define threshold voltage in digital measurements
 - f. What is the difference between Attenuator DAC and WR type DAC?
 - g. Explain the process of Quantization with suitable example

SECTION B

- 2. Attempt any three of the following: 7 x 3 = 21**
- a. Explain why the conventional method of frequency measurement is not suited for very low frequency measurement?
 - b. Give specific applications of average frequency measurements?
 - c. Draw the circuit diagram and waveforms for power system frequency measurement
 - d. What are the requirements of an ideal phase meter? Explain direct phase measurement method.
 - e. Explain Vernier technique for small time interval measurement with neat circuit diagram

SECTION C

- 3. Attempt any one part of the following: 7 x 1 = 7**
- (a) Draw the circuit diagram for minimal realizations of an inverting type PGA using dependent switching.
 - (b) What are Single Mode switching and group switching? Draw the general RS Realization of a driving point consistence in all combinations
- 4. Attempt any one part of the following: 7 x 1 = 7**
- (a) Why dB meter is used in digital measurement? Draw the circuit and explain the procedure for dB measurement.
 - (b) With suitable circuit diagram, show how fast low frequency measurement is done using frequency multiplier circuit. Also draw the waveforms.

5. Attempt any *one* part of the following: 7 x 1 = 7
- (a) Using suitable circuit diagram, explain in detail the working of weighted reference type voltage DAC
 - (b) Draw the circuit diagram of VTC using comparator and a monostable multi-vibrator and explain its working
6. Attempt any *one* part of the following: 7 x 1 = 7
- (a) Derive an expression for the total number of N-bit multistage DAC
 - (b) State and prove Sampling theorem with waveforms and explain how signal is recovered from its samples
7. Attempt any *one* part of the following: 7 x 1 = 7
- (a) Explain Time Division Multiplexing with suitable circuit scheme
 - (b) Give statement of minimum digitally PGA. Draw the minimal realization circuits using Group mode switching