

Roll No.

--	--	--	--	--	--	--	--	--	--	--	--	--

No. of Printed Pages—2

IC-603

B. TECH.

SIXTH SEMESTER EXAMINATION, 2003-2004

**ELECTRONICS MEASUREMENT &
INSTRUMENTATION**

Time : 2 Hours

Total Marks : 50

Note : Attempt **ALL** questions.1. Attempt any *FOUR* parts of the following :— (4×4=16)

- (a) Explain the working of Carey-Foster slide wire bridge.
- (b) Discuss the circuit diagram and phasor diagram of Hay's bridge. Derive the equations at balance of Hay's bridge.
- (c) Explain the factors causing errors in a.c. bridge circuits. Discuss the precautions and techniques used for reducing errors in a.c. bridges.
- (d) Describe various types of errors in instruments.
- (e) Write a short note on Storage-type Oscilloscope.
- (f) Discuss, briefly, the basic block diagram of Cathode Ray Oscilloscope. Describe horizontal deflection system in CRO.

2. Attempt any *FOUR* parts of the following :— (4×4=16)

- (a) Describe AC voltmeter using rectifier with diagram.
- (b) Discuss, briefly, electronic multimeter.
- (c) Explain vector impedance-meter with the help of block diagram.

- (d) Write a short note on True RMS reading voltmeter.
- (e) Describe the working principle of Q-meter.
- (f) Discuss the circuit for measurement of power at radio frequencies.
3. Attempt any *TWO* parts of the following :— (4·5×2=9)
- (a) Write a short note on the working of harmonic distortion-meter.
- (b) With the help of block diagram, explain spectrum analyser.
- (c) Describe Heterodyne wave-analyser with diagram.
4. Attempt any *TWO* parts of the following :— (4·5×2=9)
- (a) Explain digital energy-meter with diagram.
- (b) Describe, briefly, digital frequency-meter with diagram.
- (c) Write a short note on Time Interval Measurement.