

Printed Pages :3



\*2941 \*

101

NBC103

(Following Paper ID and Roll No. to be filled in your Answer Book)

**PAPER ID : 294103**

Roll No.

--	--	--	--	--	--	--	--	--	--

**MCA (Dual Degree) (Semester-I)**  
**SPL. THEORY EXAMINATION, 2014-15**  
**DIGITAL ELECTRONICS**

*Time : 3 Hours]**[Total Marks : 100***Note : Attempt all questions. Each question carry equal marks.**

1. Attempt any four questions.
  - A. Convert the hexadecimal number 68BE to binary, and then convert it from binary to octal.
  - B. Convert decimal 27.315 to binary.
  - C. Determine the value of base x if  $(211)_x = (152)_8$ .
  - D. Determine the 10's complement of  $(935)_{11}$ .
  - E. Discuss gray code with example.
  - F. Perform subtraction on binary numbers using 2's complement method :  $1001 - 101000$ .

2. Attempt any four questions.

- A. Demonstrate the validity of The associative law:  $x + (y + z) = (x + y) + z$  by means of truth table.
- B. Simplify the Boolean expression  $x'yz + xz$  to a minimum number of literals.
- C. Implement the Boolean function  $F = xy + x'y' + y'z$  a) with AND, OR, and inverter gates. b) with OR and inverter gates, c) with AND and inverter gates.
- D. Express the following function as a sum of minterms and as a product of maxterms:  $F(A, B, C, D) = B'D + A'D + BD$ .
- E. Show that the dual of the exclusive-OR is equal to its complement.
- F. Prove  $(x')' = x$ .

3. Attempt any two questions.

- A. Simplify the Boolean function  $F(w, x, y, z) = \sum(1, 4, 5, 6, 12, 14, 15)$  using four variable map.
- B. Simplify the following Boolean function  $F$  together with the don't-care conditions  $d$ , and then express the simplified function in sum-of-minterms form:
- $$F(x, y, z) = \sum(2, 3, 4, 6, 7)$$
- $$d(x, y, z) = \sum(0, 1, 5)$$
- C. Simplify the Boolean function  $F(A, B, C, D) = \sum(0, 2, 4, 5, 6, 7, 8, 10, 13, 15)$  using tabulation method.

4. Attempt any two questions.

- A. Show that a full adder can be constructed from two half adders and an OR gate.
- B. Design a circuit that convert a 3-bit gray code to binary code.
- C. What do you mean by decoder? Implement full adder by decoder.

5. Attempt any two questions.

- A. What do you mean by flip-flop? Discuss SR flip-flop in detail.
- B. What do you mean by shift registers? Explain Bi-directional shift register.
- C. What do you mean by counters? Discuss 3-bit binary ripple counter.

—x—