

Paper Id:

275104

Roll No:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

M. TECH.
(SEM-I) THEORY EXAMINATION 2019-20
INTRODUCTION TO ELECTRONICS & ELECTRICAL ENGINEERING

Time: 3 Hours**Total Marks: 100****Note:** Attempt all Sections. If require any missing data; then choose suitably.**SECTION A****1. Attempt all questions in brief. 2 x 10 = 20**

- a. What is the effect of negative feedback on gain in an amplifier?
- b. Write the expression for voltage gain with negative & positive feedback.
- c. What is barkhausen criterion?
- d. Why we use two transistors in a wein bridge oscillator?
- e. Write the expression for two resonant frequencies of a crystal oscillator.
- f. What is transducer?
- g. What is the purpose of resistance in the emitter circuit of a transistor amplifier?
- h. Draw the schematic symbol for SCR & TRIAC.
- i. Define quality factor of a coil.
- j. What are the universal gates? Why they are called so?

SECTION B**2. Attempt any three of the following: 10 x 3 = 30**

- (a) Describe wein bridge oscillator using OPAMP.
- (b) Explain all the regions of operation of a BJT.
- (c) Discuss common emitter amplifier.
- (d) Draw & explain the V-I characteristics of a zener diode.
- (e) Write short notes on: (i) Avalanche Breakdown (ii) Zener breakdown.

SECTION C**3. Attempt any one part of the following: 10 x 1 = 10**

- (a) Write short notes on SCR.
- (b) Describe the basic construction of BJT.

4. Attempt any one part of the following: 10 x 1 = 10

- (a) Write a technical note on inverters.
- (b) State Demorgan's theorem and prove it.

5. Attempt any one part of the following: 10 x 1 = 10

- (a) Draw the symbol & truth table of a 4 input gate if the gate is
 - (i) NAND gate.
 - (ii) OR gate
 - (iii) XOR gate
- (b) Write a shortnotes on 'IGBT'

6. Attempt any one part of the following: 10 x 1 = 10

- (a) What is CRO? Draw its block diagram & explain its working.
- (b) Write short note on Transformer.

7. Attempt any one part of the following: 10 x 1 = 10

- (a) Write a technical note on (i) Phase shift oscillator (ii) Crystal oscillator .
- (b) What is the need of biasing in transistor? Discuss the emitter biased circuit with the help of neat diagram.